



Digital Signals

W. Bolton, "Mechatronics --- Electronic control systems in mechanical and electrical engineering," 5th edition, Pearson Education Limited 2012, Chap 4
J. Edward Carryer, R. Matthew Ohline, Thomas W. Kenny, "Introduction to Mechatronic Design," Prentice Hall 2011, Chap 16, 19
線上學習網站 : <https://www.electronics-tutorials.ws>
PowerPoint 中部分圖片擷取和修改自教科書和網路圖片
機電系統原理與實驗一 ME5126 林沛群

林沛群
國立台灣大學
機械工程學系

1



Digital Signals -1

□ Function

- ◆ To represent information with logical states
 - True – ON, 1, high – a voltage close to power a device (ex: 5V, 3.3V)
 - False – OFF, 0, low – 0V
 - In a 5V device: -0.3V~1.8V Low ; 3.6V~5.5V High

□ Digital devices

- ◆ Logic devices (ex: AND, OR, NOT...)
- ◆ Microcontroller
- ◆ Programmable logic controller (PLC)
- ◆ Sensors / actuators (might be analog as well)



Digital Signals -2

❑ Timing limitations

- ◆ Input timing:
 - An upper frequency limit to how often an input signal may change states (often a few MHz)
 - Rise time & fall time (10% - 90%)
- ◆ Output timing: Real output exhibit a finite rise time and fall time
- ◆ Delays: A short propagation time occurs as the information propagates through the device
- ◆ Preparation
 - Setup time: Information at an input is required to be present and stable for a minimum amount of time
 - Hold time: the data must remain stable for a minimum amount of time

Digital Signals -3

❑ Pull-ups and pull-downs

- ◆ Floating: when a digital device input is not actively driven by the output of another device; may change states randomly
 - Electrical noise
 - Extra power consumption
- ◆ The circuit should include provisions to establish the desired state
- ◆ Method: Connecting the input with a resistor
 - To power: Pulled up
 - To ground: Pulled down


Digital Signals -4

❑ Voltage level Translator


- ◆ Solving the incompatibility between different devices supplied by different power domain

- ◆ Ex: TI TXB0104

 - Bidirectional
- Automatic Direction Sensing
- 1.2V to 3.6V on A Port
- 1.65V to 5.5V on B Port
- $V_{CC_A} \leq V_{CC_B}$



 D or PW Package
14-Pin SOIC or TSSOP
Top View



Digital Signals -5

❑ Binary Numbers

- ◆ Bit 0: Least significant bit (LSB)
- ◆ The highest bit: Most significant bit (MSB)
- ◆ Byte: 8 bits

...	2^3	2^2	2^1	2^0
...	bit 3	bit 2	bit 1	bit 0

$$15 = 1 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 1 \times 2^0$$

1111

$$12 = 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 0 \times 2^0$$

1100

Digital Signals -6

□ Number systems

Binary-coded decimal system



Decimal	Binary	BCD	Octal	Hexadecimal
0	0000	0000 0000	0	0
1	0001	0000 0001	1	1
2	0010	0000 0010	2	2
3	0011	0000 0011	3	3
4	0100	0000 0100	4	4
5	0101	0000 0101	5	5
6	0110	0000 0110	6	6
7	0111	0000 0111	7	7
8	1000	0000 1000	10	8
9	1001	0000 1001	11	9
10	1010	0000 0000	12	A
11	1011	0001 0001	13	B
12	1100	0001 0010	14	C
13	1101	0001 0011	15	D
14	1110	0001 0100	16	E
15	1111	0001 0101	17	F

Digital Signals -7

□ Parity method for error detection






- ◆ A parity bit: An extra 0 or 1 bit attached to a code group at transmission to detect the errors which alters the logical level of the signal
- ◆ Ex: $1001 \rightarrow 1101$, using “even” parity bit
 - Add 0 to an even number 01001
 - Add 1 to an odd number 11101

□ Checksum

- ◆ A block of code may be checked by sending a series of bits representing their binary sum

Analog and Digital Signals -1

□ A-to-D conversion

     

機電系統原理與實驗—ME5126 林沛群

9

Analog and Digital Signals -2


□ A-to-D conversion

- ◆ Analog full scale F_s , n -bit \rightarrow resolution $\frac{F_s}{2^n}$

□ Ex: Thermalcouple

- ◆ 0.5 mV/°C
- ◆ Measurement range
0 – 200°C
- ◆ Resolution 0.5°C

Need ?-bit ADC?

 


機電系統原理與實驗—ME5126 林沛群

10

Analog and Digital Signals -3

□ Sampling Theorem

 
- ◆ A continuous time signal can be represented in its samples and can be recovered back when sampling frequency f_s is greater than or equal to the **twice the highest frequency f_m** component of message signal $\rightarrow f_s \geq 2f_m$



機電系統原理與實驗—ME5126 林沛群

Analog and Digital Signals -4

□ Effect of sampling frequency

 

- ◆ The samples of two sine waves can be identical when at least one of them is at a frequency above half the sample rate



機電系統原理與實驗—ME5126 林沛群


Analog and Digital Signals -5

□ A-to-D conversion errors

- ◆ Quantization error, $\pm \frac{1}{2} LSB$
- ◆ Offset error: the line drawn through the midpoint of each of the steps intersects the x-axis at a location other than the origin
- ◆ Gain error: The slope of the line representing the transfer function differs from the idea slope
- ◆ Nonlinearity error

Analog and Digital Signals -6

□ D-to-A conversion

 

A-to-D and D-to-A converters -1

- ❑ PWM DAC
- ❑ Weighted-resistor DAC

- ◆ OP summing circuit


$$V_{out} = -\left(\frac{R_o}{R} bit_3 + \frac{R_o}{R} bit_2 + \frac{R_o}{R} bit_1 + \frac{R_o}{R} bit_0\right)V_{REF}$$

$$= -\frac{R_o V_{REF}}{R} (8bit_3 + 4bit_2 + 2bit_1 + 1bit_0)$$

- ◆ Ex: 4-bit conversion

- ◆ Drawback:

 - Need accurate resistors over a wide range




A-to-D and D-to-A converters -2

- ❑ R-2R ladder DAC




- ◆ Advantages

 - Easily scalable to any desired number of bits
- Uses only two values of resistors



A-to-D and D-to-A converters -3

□ Ex: ZN558D

   


機電系統原理與實驗—ME5126 林沛群

17

A-to-D and D-to-A converters -4

□ A-to-D conversion

 - ◆ Successive approximation register (SAR)
 - A faster method than the comparison starting the count at 1 and then proceeding bit by bit upward
 - n-bit word only takes n steps




機電系統原理與實驗—ME5126 林沛群

18

A-to-D and D-to-A converters -5


Ex: ZN439, an 8-bit ADC

Conversion time: $5\mu s$


 


A-to-D and D-to-A converters -6

Ramp ADC

 


Dual ramp ADC

  

A-to-D and D-to-A converters -7

□ Flash ADC

 - ◆ Very fast: n -bit converter, $2^n - 1$ separate voltage comparators used in parallel



A-to-D and D-to-A converters -8


□ ADC specifications

- ◆ Conversion time
- ◆ Resolution
- ◆ Linearity error, $\pm \frac{1}{2} LSB$

A-to-D and D-to-A converters -9

□ Sample and hold amplifier


 
- ◆ To sample the analog signal and hold it while the conversion takes place
- ◆ Switch is closed: $v_{out} = v_{in}$
- ◆ Switch is open: $v_{out} = v_{capacitor}$
- ◆ Acquisition time: the time required for the capacitor to charge to a new sample of the input analog voltage
 - Typical value, $4\mu s$



Multiplexer -1

□ Multiplexer

  
- ◆ A device that selects between several analog or digital input signals and forwards it to a single output line
 - AI sampling rate
 - Single channel, Ex: 48 kS/s
 - Multi channels (aggregate)
 - One channel 48 kS/s
 - n channels $\rightarrow \frac{48}{n}$ kS/s




Multiplexer -2

Digital Multiplexers

- Ex: a two-input example

 


 - Ex: 151 types
 - Enable one line from eight




Multiplexer -3

 - Ex: 153 types
 - Enable one line from four inputs which are supplied as data on two lines each




 - Ex: 157 types
 - Enable one line from two inputs which are supplied as data on four lines each



Multiplexer -4


□ Time division multiplexer

 

Data Acquisition (DAQ)


□ DAQ

 - ◆ Used for the process of taking data from sensors and inputting that data into a computer for processing




□ Direct memory access (DMA)

 - ◆ A feature of computer systems that allows certain hardware subsystems to access main system memory (random-access memory), independent of the central processing unit (CPU)



NI myRIO 1900 - 1

□ Specifications

 

NI myRIO 1900 - 2

□ Block diagram and connectors

Figure 3. Primary/Secondary Signals on MXP Connectors A and B


 
 


Figure 4. Primary/Secondary Signals on MSP Connector C

 

NI myRIO 1900 - 3

◆ Digital IO

- Channels: 16 (MXP) x2; 8 (MSP)
- 3.3V output;
- 3.3V / 5V-compatible input
- When a DIO line is floating, it floats in the direction of the pull resistor
 - Starting up
 - Configured as input
 - Powering down
- Secondary digital functions
 - Serial peripheral interface bus (SPI)
 - Pulse-width modulation (PWM)
 - Quadrature encoder input
- UART TX/RX: identical to DIO 0-13

Figure 7. DIO Lines <13..0> on MXP Connector A or B

 


Figure 8. DIO Lines <15..14> on MXP Connector A or B


 



Figure 9. DIO Lines <7..0> on MSP Connector C

 

NI myRIO 1900 - 4


◆ Analog input

 
- Channels: 4 (MXP, single ended) x2; 2 (MSP, differential)
- Aggregate sampling rate: 500 kS/s
- Resolution: 12 bits
- Nominal range: 0 V to + 5 V (MXP); ±10V (MSP)



◆ Analog output

 - Channels: 2 (MXP) x2; 2 (MSP)
- Aggregate sampling rate: 345 kS/s
- Resolution: 12 bits
- Nominal range: 0 V to + 5 V (MXP); ±10V (MSP)
- Slew rate: 0.3 V/μs (MXP); 2 V/μs (MSP)



 

終

□ Questions?

