



## Signal Conditioning

W. Bolton, "Mechatronics --- Electronic control systems in mechanical and electrical engineering," 5<sup>th</sup> edition, Pearson Education Limited 2012, Chap 3  
J. Edward Carryer, R. Matthew Ohline, Thomas W. Kenny, "Introduction to Mechatronic Design," Prentice Hall 2011, Chap 11 & 12  
線上學習網站 : <https://www.electronics-tutorials.ws>  
PowerPoint 中部分圖片擷取和修改自教科書和網路圖片  
機電系統原理與實驗一 ME5126 林沛群

林沛群  
國立台灣大學  
機械工程學系

1

## Signal Conditioning -1

### □ Goal

- ◆ The output signal from the sensor of a measurement system has generally to be processed in some way to make it suitable for the next stage of the operation

# Signal Conditioning -2

## ❑ Process

- ◆ **Protection:** To prevent damage to the next element
  - Ex: Microprocessors - current & voltage limitations
- ◆ Getting the signal into the **right type** of signal
  - Ex: AC-DC conversion, AD-DA conversion
- ◆ **Amplification & Offset**
  - Ex: Wheatstone bridge (voltage amplification)
- ◆ **Noise elimination** or reduction
  - Ex: Filters
- ◆ **Signal manipulation**
  - Ex: Conditioner to linearize the signal

# Protection -1

## ❑ High current



- ◆ Incorporating **a series resistor** in the input line to limit the current
- ◆ Incorporating **a fuse** to break if the current does exceed a safe level

## ❑ High voltage & wrong polarity


- ◆ Zener diode circuit

- Ex: for a 5V circuit

Choose a 5.1V Zener diode

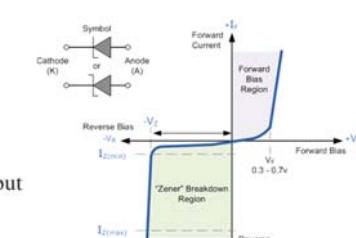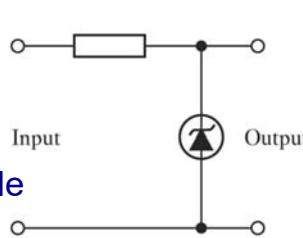

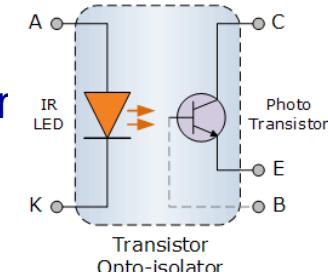
## ❑ Complete electrical isolation – opto-coupler



## Protection -2

### □ Combined

for alternating signal in the input

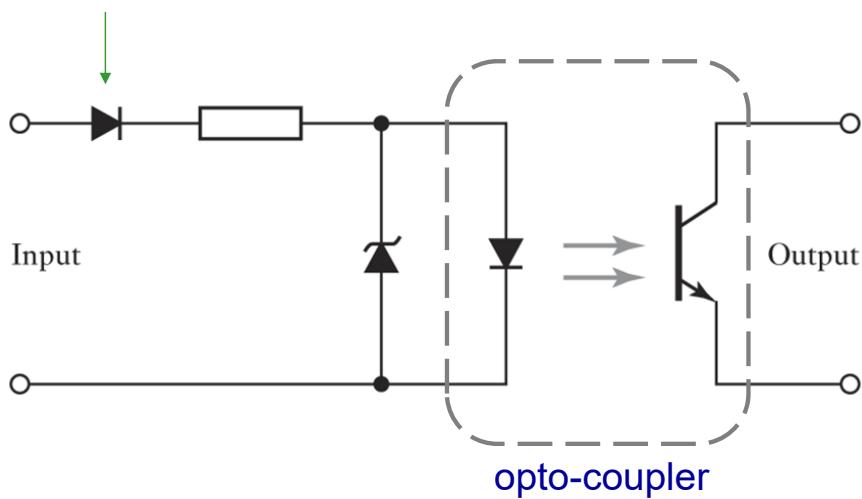

## Amplifier -1

### □ Definition

- ◆ Describe a circuit which produces an increased version of its input signal


### □ Three kinds

- ◆ Voltage gain ( $A_v$ )
- ◆ Current gain ( $A_i$ )
- ◆ Power gain ( $A_p = A_v \times A_i$ )
- ◆ Can be represented in dB

$$\circ A_v = 20 \log(A_v)$$

$$\circ A_i = 20 \log(A_i)$$

$$\circ A_p = 10 \log(A_p)$$

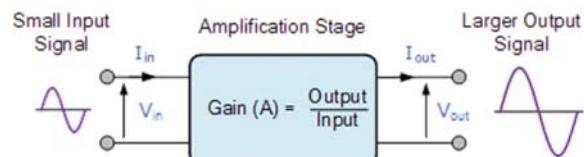

## Amplifier -2

### □ Ideal amplifier

- ◆ Constant gain, independent of
  - Input signal conditions
  - Temperature
  - Time

### □ Components

- ◆ BJT
- ◆ MOSFET
- ◆ Operational amplifier

## Complex (Electrical) Impedance -1

### □ Definition


- ◆ The measure of the opposition that a circuit presents to a current when a voltage is applied
- ◆ Quantitatively, the impedance of a two-terminal circuit element is the **ratio** of the complex representation of a sinusoidal **voltage** between its terminals to the complex representation of the **current** flowing through it

$$Z = R + jX = |Z|e^{j\arg(Z)}$$

$$Z \triangleq \frac{V}{I}$$

## Complex (Electrical) Impedance -2

### □ Computation – circuit

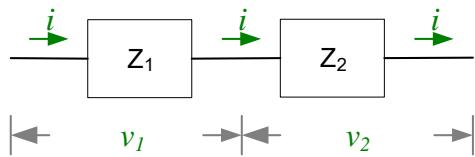


Current  $i$  : the same

$$V_1 = IZ_1 \quad V_2 = IZ_2$$

$$V = V_1 + V_2 = IZ_1 + IZ_2 = I(Z_1 + Z_2) = IZ \quad Z = Z_1 + Z_2$$

- ◆ Series and parallel laws applicable

- ◆ NOT transfer function

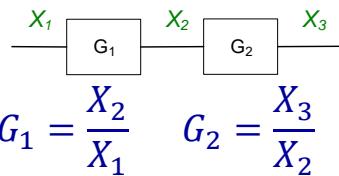

$$G = \frac{X_3}{X_1} = \frac{X_2}{X_1} \frac{X_3}{X_2} = G_1 G_2 \quad G = G_1 G_2$$

## Complex (Electrical) Impedance -3

### □ Passive components

- ◆ Resistor



$$v = iR$$

$$Z_R = \frac{V}{I} = R$$

- ◆ Capacitor



$$i = C \frac{dv}{dt}$$

$$Z_C = \frac{V}{I} = \frac{1}{Cs}$$

- ◆ Inductor



$$v = L \frac{di}{dt}$$

$$Z_L = \frac{V}{I} = Ls$$


# The Operational Amplifier -1

## □ Definition


- ◆ A DC-coupled high-gain electronic voltage amplifier with a differential input and, usually, a single-ended output
- ◆ Voltage gains  $\sim 100000$

## □ Two Golden Rules

- ◆  $i_1 = i_2 = 0$
- ◆  $v_1 = v_2$

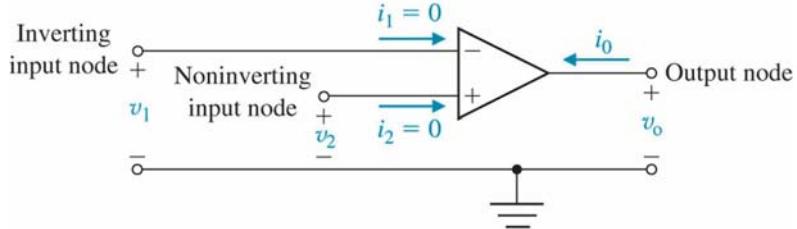

## □ Ex: OP741

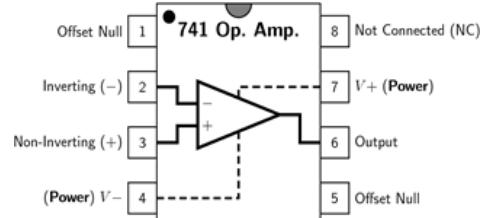

機電系統原理與實驗—ME5126 林沛群

11

# The Operational Amplifier -2

## □ Inverting amplifier

- ◆ Resistors

$$\circ \quad v_- = v_+ = 0$$


$$\circ \quad i = \frac{v_{in} - v_-}{R_1} = \frac{v_{in}}{R_1}$$

$$\circ \quad v_0 = v_- - R_2 i = -\frac{R_2}{R_1} v_{in}$$

$$\rightarrow \quad G = \frac{v_0}{v_{in}} = -\frac{R_2}{R_1}$$

- Inverter, if  $R_1 = R_2$
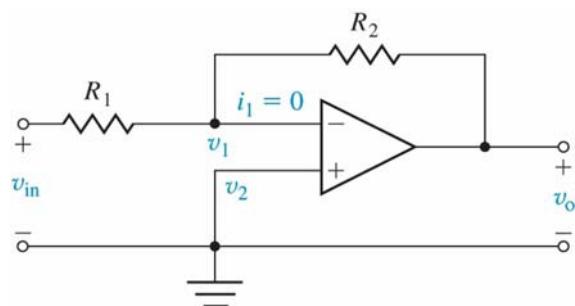
$$\rightarrow \quad G = \frac{v_0}{v_{in}} = -1$$



機電系統原理與實驗—ME5126 林沛群

12


# The Operational Amplifier -3

## □ Inverting amplifier

- ◆ Impedance – in Laplace domain

$$\Rightarrow G(s) = \frac{V_{out}(s)}{V_{in}(s)} = -\frac{Z_2}{Z_1}$$

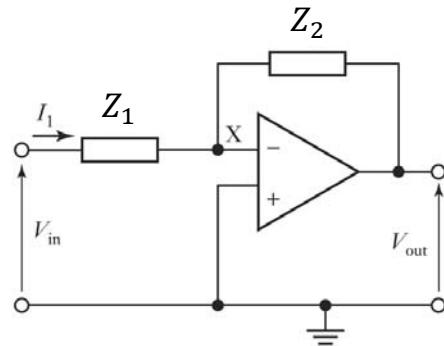- For general passive components
  - Ex: resistors, capacitors, inductors





# The Operational Amplifier -4


- ◆ Summing amplifier

$$V_{out} = -\left(\frac{R_2}{R_A} V_A + \frac{R_2}{R_B} V_B + \frac{R_2}{R_C} V_C\right)$$

- Ex: Offset the output

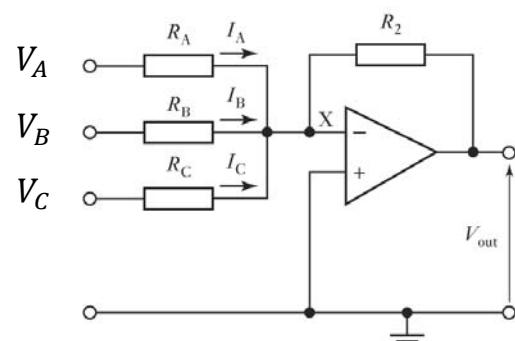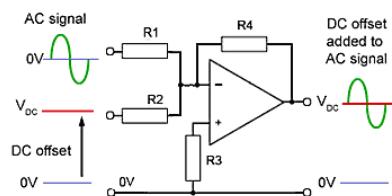


- Ex: Weighted sum -> D-to-A converter

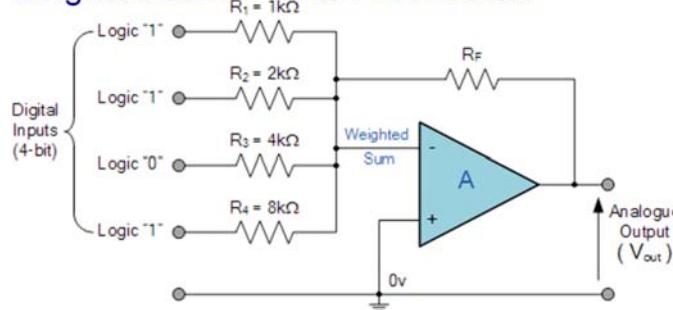

# The Operational Amplifier -5

- ◆ (Non-inverted) summing amplifier

- Adding an inverter

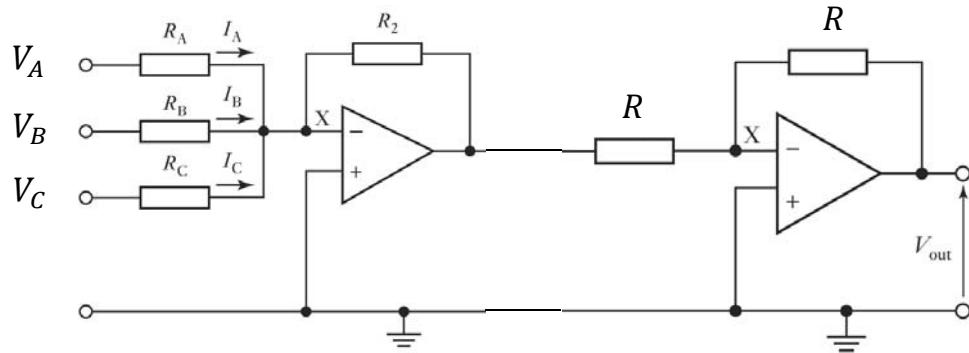

$$V_{out} = \frac{R_2}{R_A} V_A + \frac{R_2}{R_B} V_B + \frac{R_2}{R_C} V_C$$

- How to build a subtractor?


# The Operational Amplifier -6

- ◆ Integrating amplifier


$$V_{out}(s) = -\frac{1}{RCs} V_{in}(s)$$

- ◆ Differentiating amplifier

$$V_{out}(s) = -RCsV_{in}(s)$$

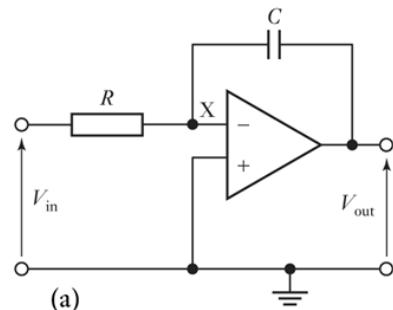

(a)

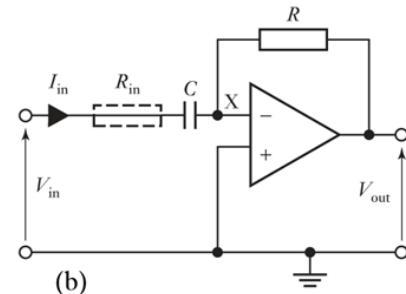

(b)


## The Operational Amplifier -7

### □ Non-inverting amplifier

- ◆  $V_{out} = V_- + Z_2 I = V_+ + Z_2 \frac{V_+}{Z_1}$

$$= \left(1 + \frac{Z_2}{Z_1}\right) V_{in} = G V_{in}$$

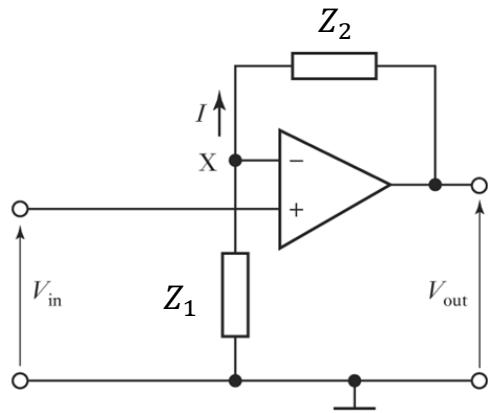
➡  $G = \frac{V_{out}(s)}{V_{in}(s)} = 1 + \frac{Z_2}{Z_1}$



### □ Voltage follower

- ◆ If  $Z_2 \rightarrow 0$  and  $Z_1 \rightarrow \infty$

➡  $G \rightarrow 1$

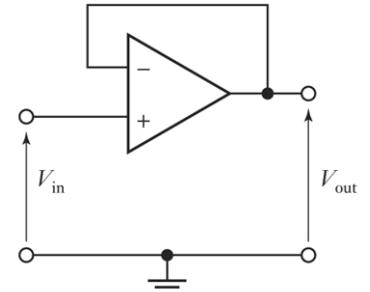

## The Operational Amplifier -8

### □ Differential amplifier

#### ◆ Impedance

- $V_+ = \frac{Z_4}{Z_3 + Z_4} V_2 = V_-$


- $V_{out} = V_- - \frac{V_1 - V_-}{Z_1} Z_2$

➡  $V_{out} = \frac{Z_1 + Z_2}{Z_1} \frac{Z_4}{Z_3 + Z_4} V_2 - \frac{Z_2}{Z_1} V_1$

- If  $Z_3 = Z_1$  and  $Z_4 = Z_2$  ➡  $V_{out} = \frac{Z_2}{Z_1} (V_2 - V_1) = G_{diff} \Delta V$

- Set  $V_{ref} = \frac{Z_4}{Z_3 + Z_4} V_2$

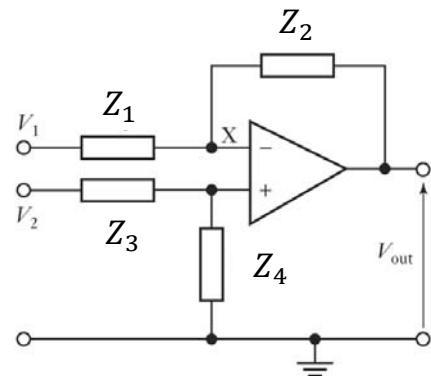➡  $V_{out} = \frac{Z_1 + Z_2}{Z_1} V_{ref} - \frac{Z_2}{Z_1} V_1 = \frac{Z_2}{Z_1} (V_{ref} - V_1) + V_{ref}$



small input signal  
gain

offset

## The Operational Amplifier -9

- Empirically, common mode voltage may affect the output

- $V_{out} = G_{diff} \Delta V + G_{CM} V_{CM}$
- Common mode rejection ratio (CMRR) =

$$\frac{G_{diff}}{G_{CM}} \text{ (dB)}$$

- Ex: 10000  $\rightarrow 20 \log 10000 = 80 \text{ (dB)}$

## The Operational Amplifier -10

- Ex: Thermalcouple (measuring)


- Advantages

- Low cost
- Accurate and repeatable
- Wide temperature range
- Reliable
- Easy to setup



- Disadvantages

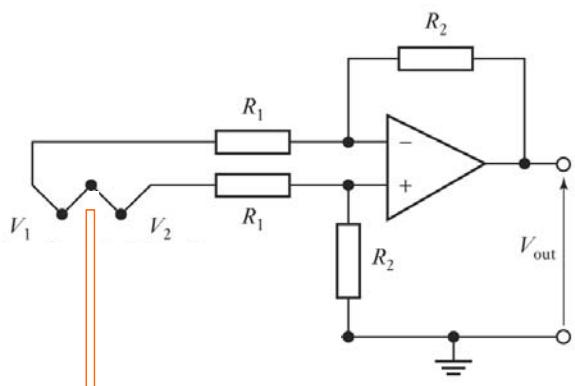
- Time constant: a function of wire mass
- Small output voltage
- Need electrical insulation



$$V = \int_{T_{ref}}^{T_{sense}} (S_+(T) - S_-(T)) dT$$

$S_+$ ,  $S_-$ : Seebeck coefficients

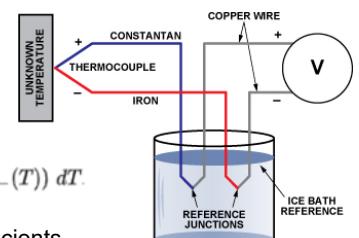
Also need to know  $T_{ref}$  (cold junction compensation)



# The Operational Amplifier -11
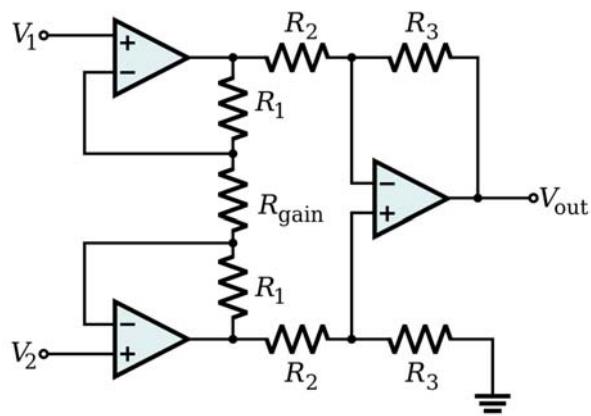
## Instrumentation amplifier

- ◆ High input impedance
- ◆ High gain
- ◆ Excellent CMRR
  - >100 dB





$$\frac{V_{out}}{V_2 - V_1} = G = \frac{R_3}{R_2} \left(1 + \frac{2R_1}{R_{gain}}\right)$$

# The Operational Amplifier -12

## Instrumentation amplifier

- ◆ Ex: INA114

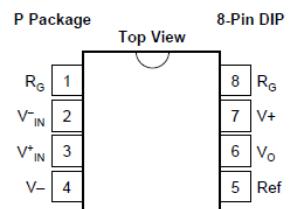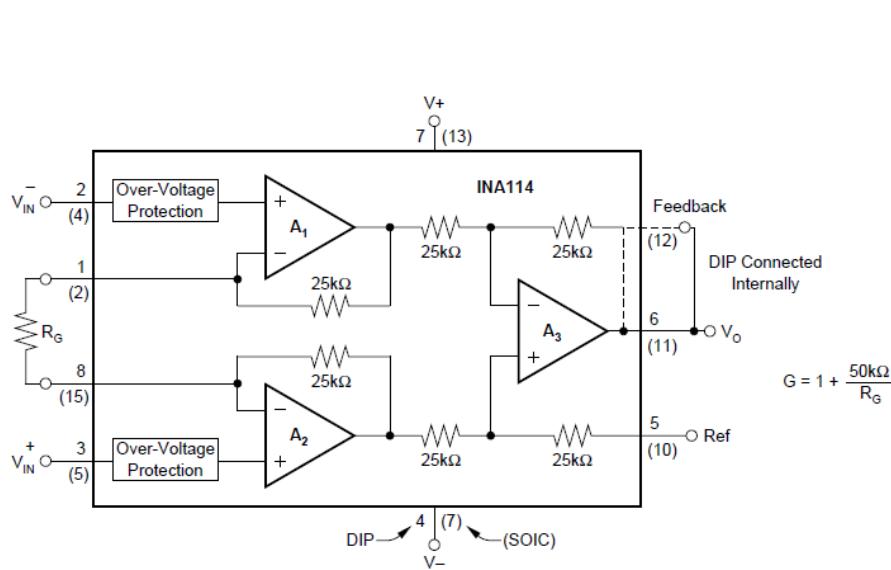

Input impedance, differential common mode:  $10^{10} \Omega$  in parallel with 6 pF

Input common mode range:  $\pm 13.5$  V

Common mode rejection,  $G = 1:90$  dB,  $G = 1000:110$  dB




Gain range 1 to 10,000

Gain error: 2% max.

Output voltage:  $\pm 13.7$  V ( $V_s = \pm 15$  V)

# The Operational Amplifier -13

## □ Comparator

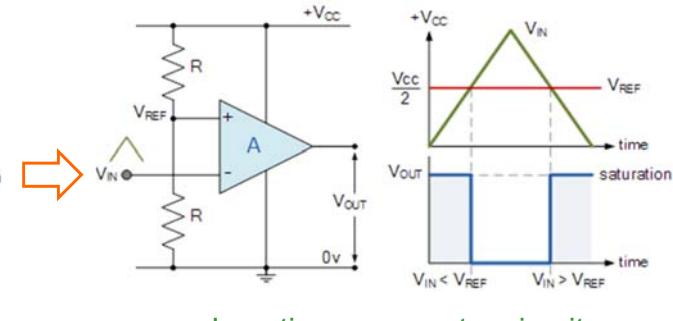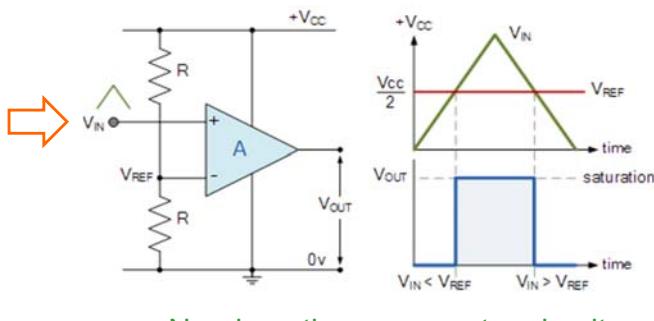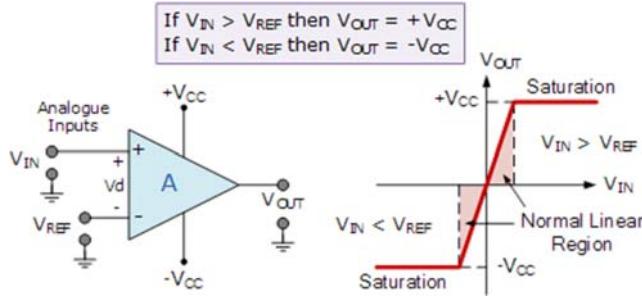


機電系統原理與實驗—ME5126 林沛群

23


# The Operational Amplifier -14

## □ Window comparator

### ◆ Method 1

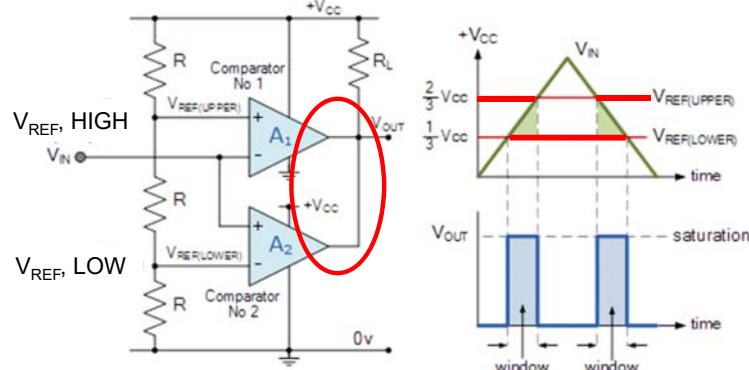

### ◆ Method 2

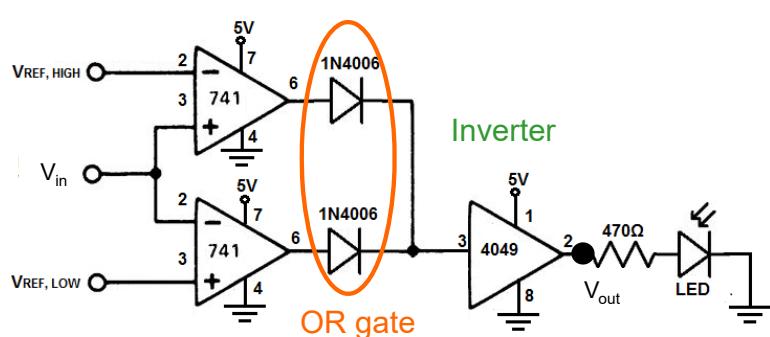


From <http://www.learningaboutelectronics.com>

機電系統原理與實驗—ME5126 林沛群

24

# The Operational Amplifier -15

## □ Comparator – reference voltage

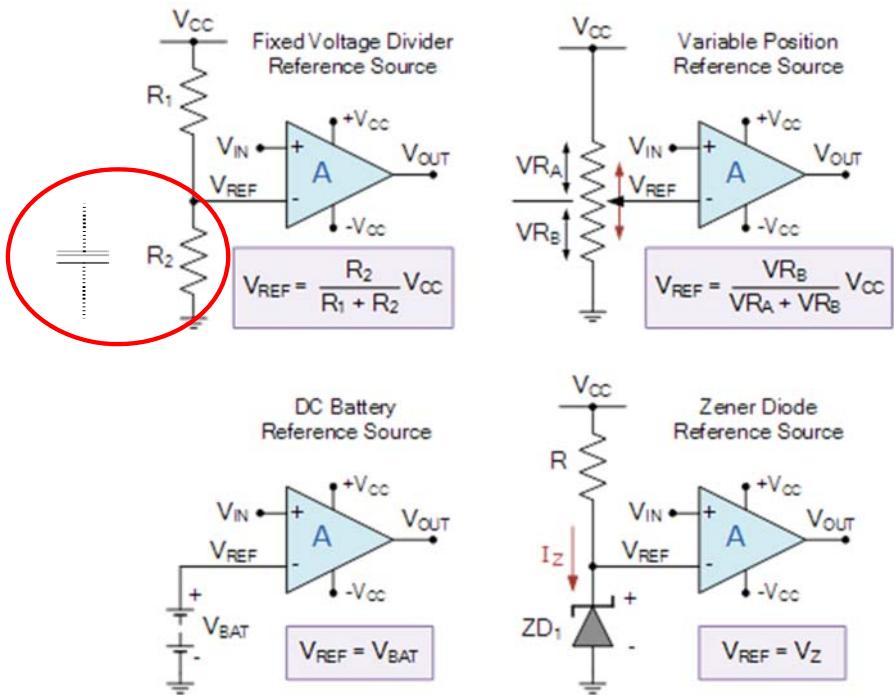


# The Operational Amplifier -16

## □ Comparator – voltage level detector

- ◆ Five levels:  $0.2V_{cc}$        $0.4V_{cc}$        $0.6V_{cc}$        $0.8V_{cc}$        $V_{cc}$
  - ◆ Five resistors
  - ◆ Four reference voltages
- LEDs are labeled  $LED_4$  and  $LED_1$  corresponding to the lowest and highest reference voltages respectively.
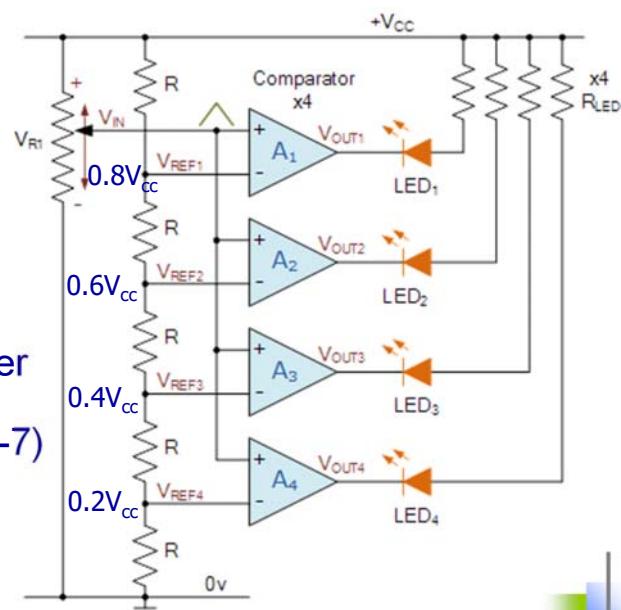
## □ 3-bit ADC


- ◆ 7 Ops + 8-to-3 line digital decoder
- ◆ Analog → 3-bit binary code (0-to-7)



# The Operational Amplifier -17
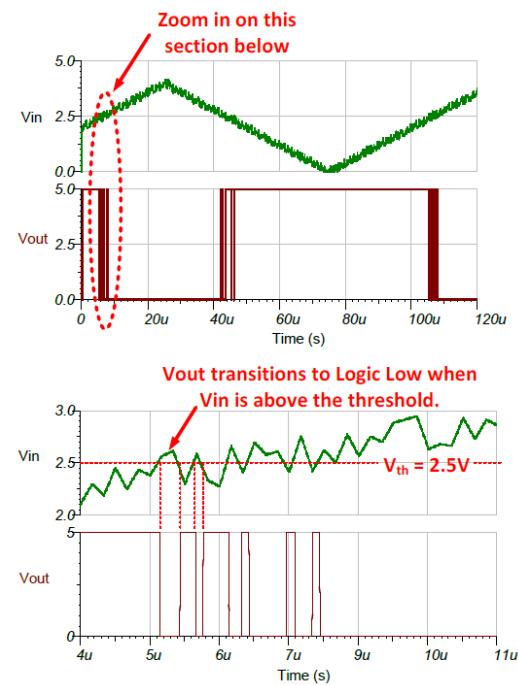
## □ Comparator with hysteresis



- ◆ Original open-loop design
  - If the input signal varies rapidly: fine
  - If the input signal varies slowly or the noise exists: Oscillating switching back and forth between the two saturation states



# The Operational Amplifier -18

## □ Comparator with hysteresis

- ◆ Closed-loop design

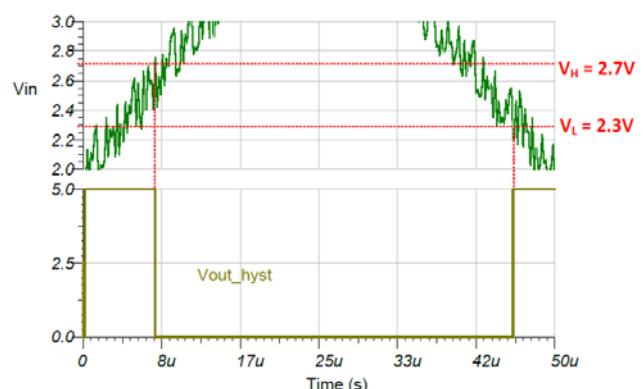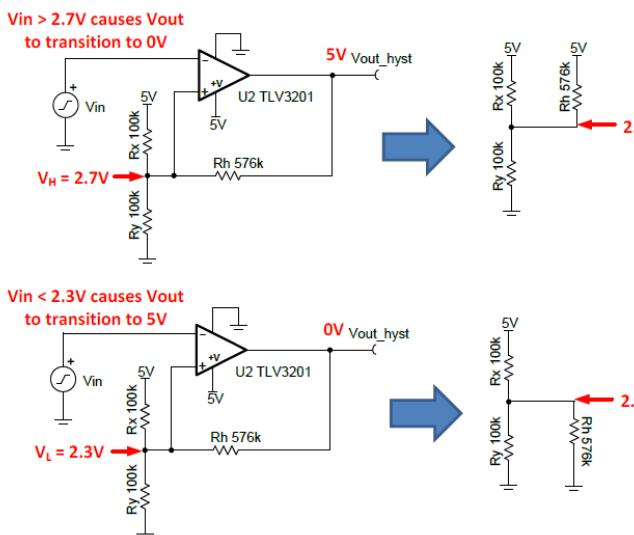

# The Operational Amplifier -19

## ❑ Notes


- ◆ Ops are optimized for linear operation, not in saturation mode
- ◆ Dedicated voltage comparator: Allows for heavy saturation, due to its very high gain, when the input signals differs by a relatively small amount
- ◆ Ex: LM311, LM339, LM393...

# The Operational Amplifier -20

## ❑ Transimpedance amplifier

- ◆ A current to voltage converter

$$\Rightarrow V_{out} = -R_f I_{in}$$

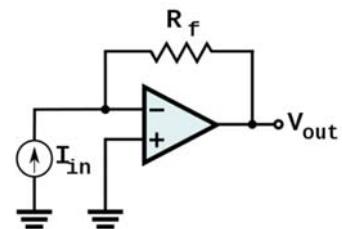

# Wheatstone Bridge -1



## □ Definition

- ◆ A combination of four resistances connected to give a null center value
- ◆ Interfacing various transducers and sensors to the amplifier circuits
- ◆ Input vs. output =?
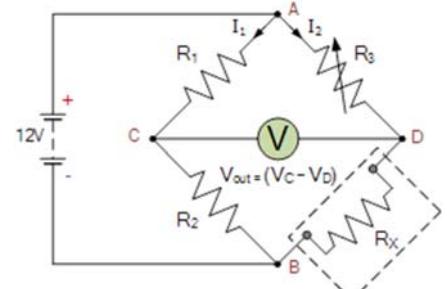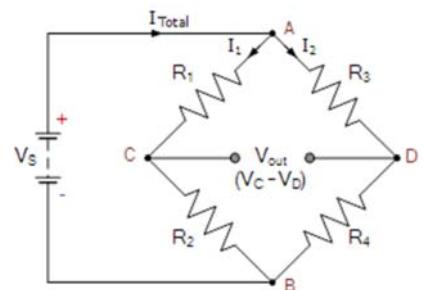
## □ Wheatstone bridge circuit

- ◆  $R_x$ : sensing
- ◆  $R_3$ : “balance” the bridge


$$\frac{R_1}{R_2} = \frac{R_3}{R_x} = 1$$




# Wheatstone Bridge -2
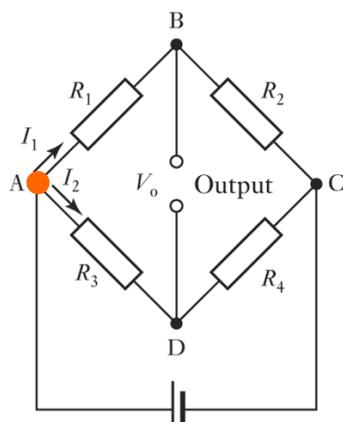
## □ Lead compensation

- ◆ If the sensing element is at the end of a long lead
  - Original form: temperature change matters
  - Three-lead form: “temperature compensation”
    - Line 1:  $R_1 \rightarrow R_3$



Original form

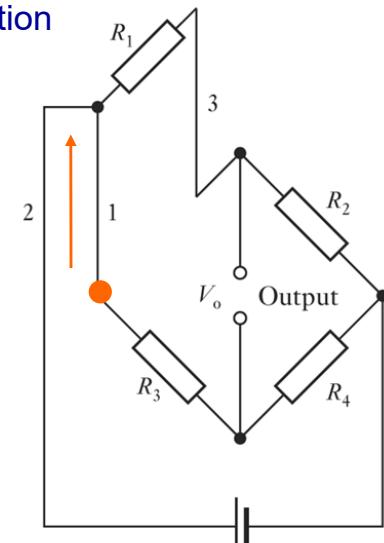


Three-lead form

## Wheatstone Bridge -3
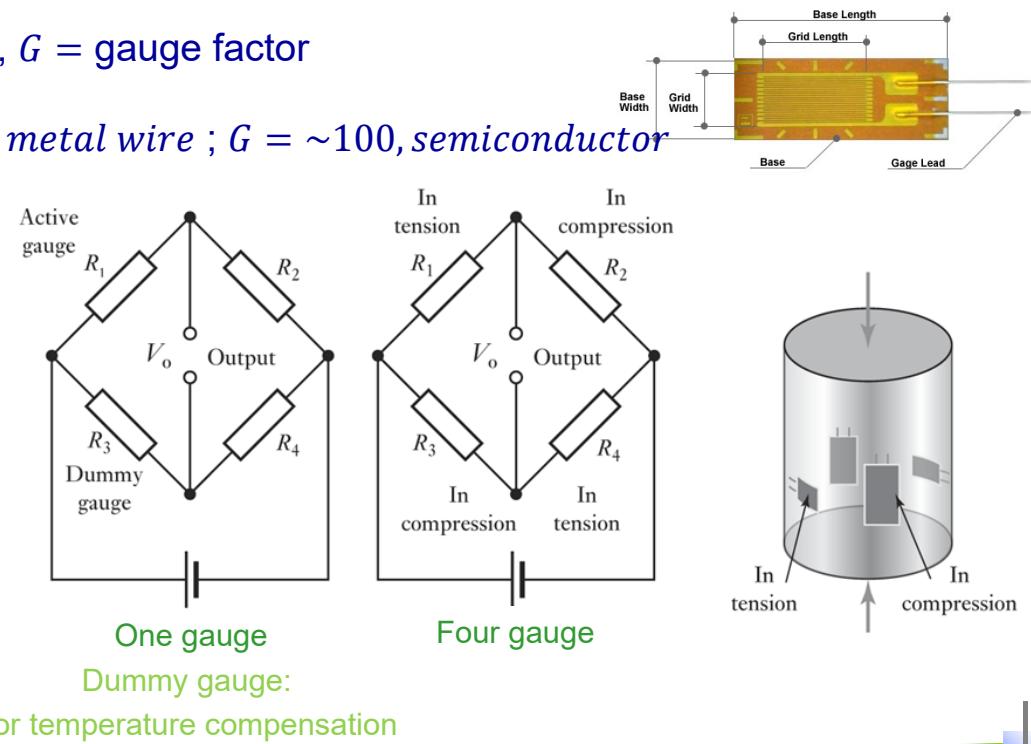
### □ Ex: Strain gauges


- ◆  $\frac{\Delta R}{R} = G\varepsilon$ ,  $G$  = gauge factor
- ◆  $G = \sim 2$ , metal wire ;  $G = \sim 100$ , semiconductor



## Wheatstone Bridge -4
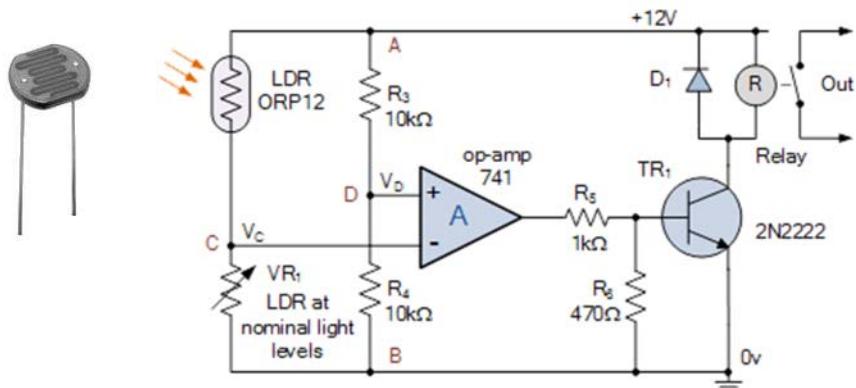
### □ Ex: Wheatstone bridge light detector

- ◆ Bridge + OP comparator
- ◆ LDR: Light dependent resistor
- ◆  $VR_1$ : Balance the bridge circuit at the required light intensity
- ◆ Ex: ORP12,  $R = 10M\Omega$  (dark)  $\rightarrow 100\Omega$  (light)



# Wheatstone Bridge -5


## □ Ex: Wheatstone bridge air conditioner

- ◆ Bridge + OP comparator

- ◆ Thermistor

- Ex:  $10\text{K}\Omega$  at  $25^\circ\text{C}$  and  $100\Omega$  at  $100^\circ\text{C}$

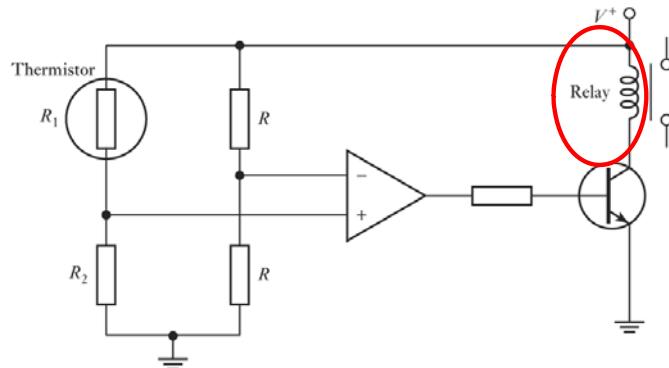- ◆ Temperature  $\uparrow$ ;  $R_1 \downarrow$ ;  $V_+ \uparrow$ ; OP ON; NPN saturated





# Filtering -1




## □ Definition

- ◆ The process of removing a certain band of frequencies from a signal and permitting others to be transmitted

## □ Pass band

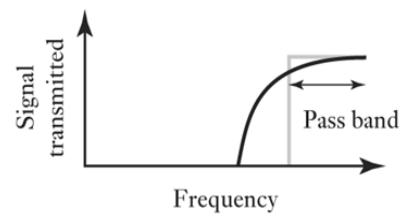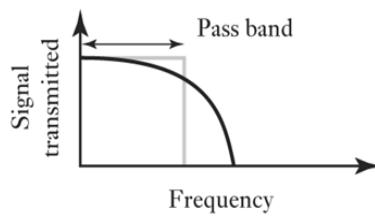
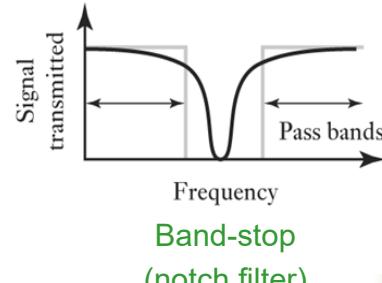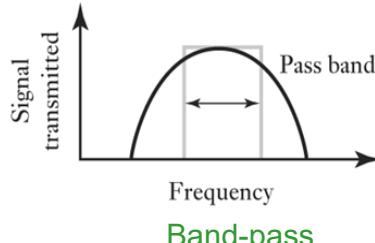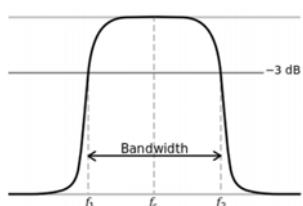
$$\text{Quality factor: } Q = \frac{f_c}{f_2 - f_1}$$




## Filtering -2

### □ Composition

- ◆ Passive: using resistors, capacitors, and inductors
  - Disadvantage: The current drawn by the output may change the frequency characteristics of the filter
- ◆ Active: Using OP

$$G(s) = \frac{1}{1 + RCs}$$

- ◆ Ex: a low-pass filter

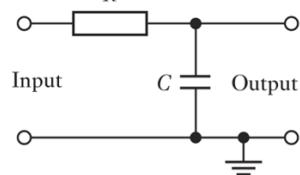

### □ Goal: High signal to noise ratio (SNR) (in dB)

## Filtering -3


### □ Frequency Response: The steady-state response of the system to a sinusoidal input

A well-studied periodic signal readily available in many instruments

input → (Stable) linear system,  $T(s)$  → output

$$r(t) = A \sin(\omega t)$$

$$y(t) = A|T(j\omega)| \sin(\omega t + \phi)$$

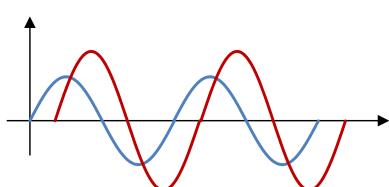

$$\phi = \angle T(j\omega)$$

Input vs. output  
Same frequency  
Different amplitude & phase angle

### □ How to obtain $T(j\omega)$ ? $\Rightarrow T(j\omega) = T(s)|_{s=j\omega}$

## Filtering -4


- Ex: A RC circuit (low-pass filter)

$$G(s) = \frac{V_c}{V_R + V_c} = \frac{\frac{I}{Cs}}{RI + \frac{I}{Cs}} = \frac{1}{RCs + 1}$$

$$\begin{aligned} G(j\omega) &= \frac{1}{j\omega(RC) + 1} = \frac{1}{j(\omega/\omega_1) + 1} = \frac{1 - j(\omega/\omega_1)}{(\omega/\omega_1)^2 + 1} \quad \tau = RC, \omega_1 = \frac{1}{RC} \\ &= \frac{1}{(\omega/\omega_1)^2 + 1} + j \frac{-(\omega/\omega_1)}{(\omega/\omega_1)^2 + 1} \quad \text{a circle centered at } (\frac{1}{2}, 0) \end{aligned}$$


$$|G(\omega)| = \frac{1}{\sqrt{1 + (\omega/\omega_1)^2}} \quad \phi(\omega) = \tan^{-1}(-\frac{\omega}{\omega_1}, 1) \quad \text{Trajectory in the 4th quadrant}$$

	$R(\omega)$	$X(\omega)$	$ G(\omega) $	$\phi(\omega) =$
$\omega = 0$	1	0	1	0
$\omega = \omega_1$	$\frac{1}{2}$	$-\frac{1}{2}$	$\frac{1}{\sqrt{2}}$	$-45^\circ$
$\omega \rightarrow \infty$	0	0	0	$-90^\circ$

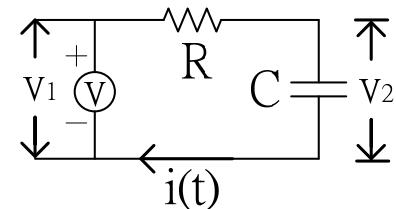

$$V_R = RI$$

$$V_C = \frac{I}{Cs}$$

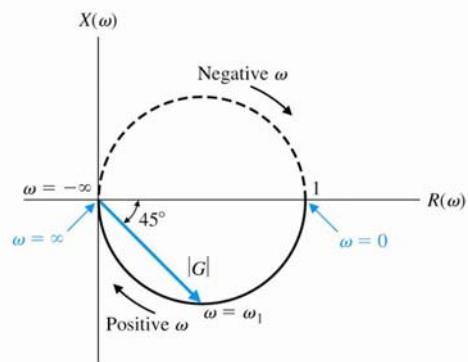

## Filtering -5

$$G(j\omega) = G(s) \Big|_{s=j\omega} = \frac{1}{RCs + 1} \Big|_{s=j\omega} = \frac{1}{j\omega\tau + 1} \quad \tau = RC$$

$$\begin{aligned} G_{dB}(\omega) &= 20 \log |G(\omega)| = 20 \log \left( \frac{1}{1 + (\omega\tau)^2} \right)^{\frac{1}{2}} \\ &= -10 \log(1 + (\omega\tau)^2) \end{aligned}$$



$$\omega \ll \frac{1}{\tau} \quad G_{dB}(\omega) = -10 \log(1) = 0 \text{ dB}$$

$$\omega = \frac{1}{\tau} \quad G_{dB}(\omega) = -10 \log(2) = -3.01 \text{ dB}$$

$$\omega \gg \frac{1}{\tau} \quad G_{dB}(\omega) = -20 \log(\omega\tau)$$

$$= -20 \log(\tau) - 20 \log(\omega)$$
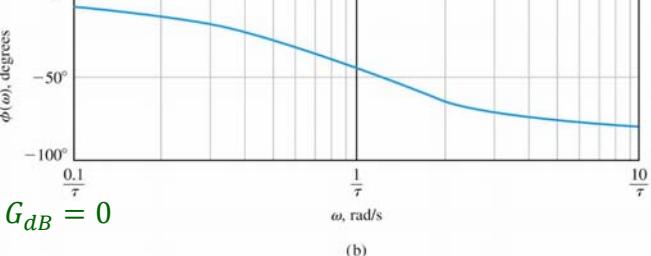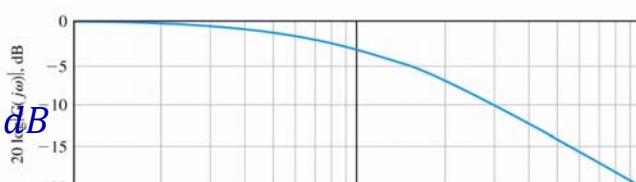
$$\phi(\omega) = -\tan^{-1} \omega\tau \quad \text{When } \omega = \frac{1}{\tau}, G_{dB} = 0$$




# Peak Detection

## □ Two methods

- ◆ In microprocessor (software), suitable for low-frequency signals
- ◆ In circuit, good for high-frequency signals


ESP

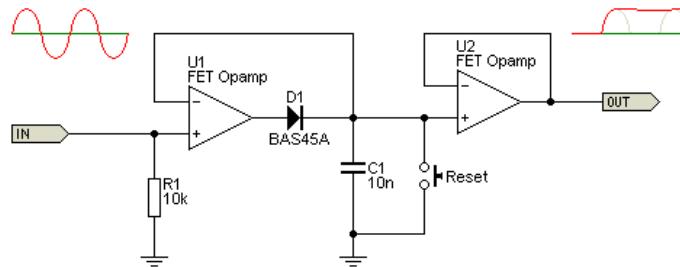



# Problems with Signals -1
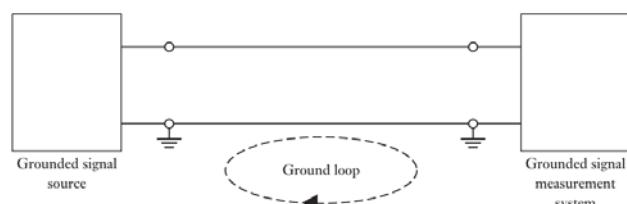
## □ Ground loop

- ◆ Occurring when two points of a circuit both intended to be at ground reference potential have a potential between them
- ◆ A major cause of noise, hum, and interference in audio, video, and computer systems



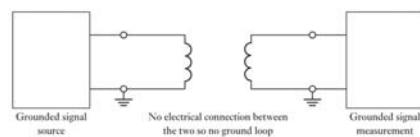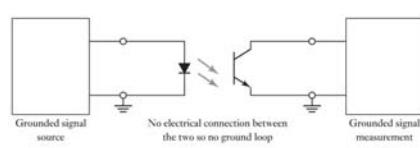
- ◆ Solution: Electrical isolation
  - Ex: opto-coupler, transformer




# Problems with Signals -2
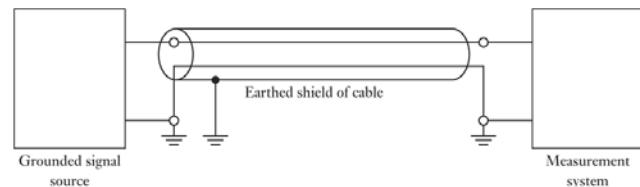
## □ Electromagnetic interference

- ◆ Resulting from time-varying electric and magnetic fields
- ◆ Ex: motors, relay coils, fluorescent lamps...
- ◆ Occurring as a result of mutual capacitance between neighboring conductors



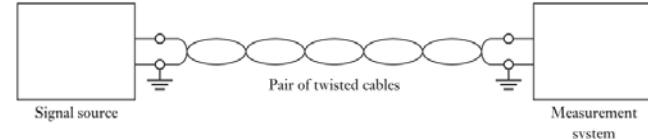- ◆ Solution: Electric shielding, Use of twisted pairs of wires for interconnections



End

## □ Questions?

